

Scalar Quantity

Current Electricity

Current Electricity

S.I unit **Ampere** or **C/s** (coulomb per sec)

Avg Current $\rightarrow \frac{\text{Total Charge}}{\text{Total time}}$ i.e. $\frac{\Delta q}{\Delta t}$ or $\frac{dq}{dt}$ \rightarrow instantaneous current at any instant

Speed of e^- on a conductor $\rightarrow 10^6 \text{ m/s}$, Avg displacement of e^- is zero (0).

Relaxation Time has no contribution in current.
is the avg time between the 2 successive collisions.

Drift velocity (v_d) is the avg rate at which free e^- are displaced against the E.f. in the order of 1 Mm/s .

depends upon:-
→ temperature
→ material

→ $T_{\text{emp}} \uparrow, kE \uparrow, T \downarrow, v_d \downarrow, \mu \downarrow$


Resistance, Resistivity and Conductivity

$R = \frac{\rho l}{A}$, $\rho = \frac{m}{ne^v I}$

$$\rho = \frac{1}{\sigma} \rightarrow \text{Conductivity}$$

Ohm's Law

$$V = IR$$

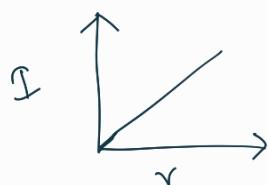

$\boxed{\text{Temp} \uparrow, kE \uparrow, T \downarrow, \sigma \uparrow, R \uparrow}$

$$\boxed{\textcircled{*} I = ne a v_d} \rightarrow 1.6 \times 10^{-19} \text{ C} \rightarrow \text{Area} \rightarrow \text{drift velocity}$$

no. of free e^- carriers per volume

in the direction of current

1 to the direction of current.

depends upon :- material, temperature
doesn't depend upon geometry

$\textcircled{*} \text{Temp} \uparrow, kE \uparrow, T \downarrow, \sigma \uparrow, R \uparrow$

Empirical Relation b/w S and Temp

$$S = S_0 (1 + \alpha \Delta T), \text{ when } \Delta T < 100^\circ\text{C}.$$

$$S_f = S_0 e^{\alpha \Delta T}, \text{ when } \Delta T > 100^\circ\text{C}.$$

Current Density

$$J = \frac{I}{A}.$$

Cell



$$\boxed{V_A - V_B = iR}$$

$$\boxed{P = \frac{V^2}{R}}$$

short circuit :-
means $i=0, V=0, R=0$.

$$\boxed{V_1 = \frac{R_1}{R_1+R_2} V, V_2 = \frac{R_2}{R_1+R_2} V}$$

Series Connection :-

$$R_{eq} = R_1 + R_2 \dots$$


Parallel Connection

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \dots$$

$$\boxed{i_1 = \frac{R_2}{R_1+R_2} I}$$

$$\boxed{i_2 = \frac{R_1}{R_1+R_2} I}$$


Wheatstone Bridge :-

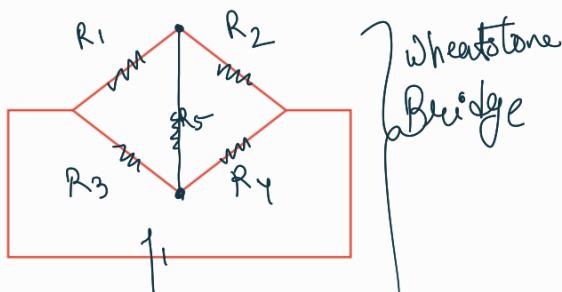

$$\text{if and only, } \frac{R_1}{R_3} = \frac{R_2}{R_4},$$


then it is called a balanced wheatstone bridge.

Terminal Voltages

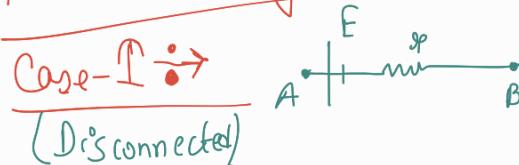

$$\Rightarrow V_A - V_B = Emf$$

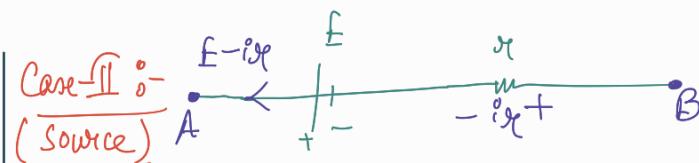
$$\Rightarrow \text{Terminal Voltage} = Emf$$



Terminal Voltage

$$\boxed{V_A - V_B = E - ir} = (E - ir) : = E_i - \frac{ir}{R}$$

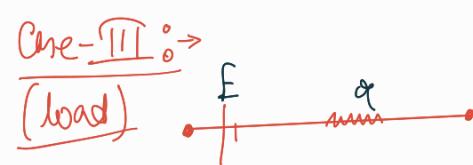
Cost dissipation due to internal resistance



Terminal Voltage,

$$V_A - V_B = E + ir$$

$$P = (E + ir)i = Ei + i^2 r$$

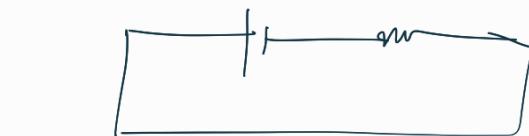

$$i = \frac{E}{r}$$

$$V_A - V_B = E - ir = E - E = 0$$

Combination of Cells →

Series Combination

$$E_{eq} = E_1 + E_2 + \dots$$


$$R_{eq} = R_1 + R_2 + \dots$$

If anyone is in opposite polarity then, it will get -ve.

If 'm' identical cells.

$$E_{eq} = mE, R_{eq} = mR.$$

Case → I

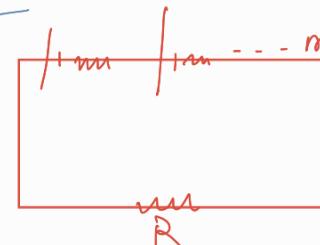


$$i = \frac{mE}{mR + R}$$

Parallel combination of cell

$$E_{eq} = \frac{\frac{1}{E_1} + \frac{1}{E_2} + \dots}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$$

* If 'n' identical cells.

$$i = \frac{nE}{nR + R}$$

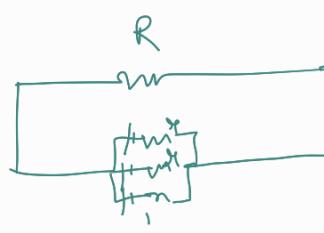

Grids of Cells →

$$E_{eq} = \frac{m}{n} E.$$

$$R_{eq} = \frac{m}{n} R.$$

$$i = \frac{mE}{R + \left(\frac{mR}{n}\right)}$$

$$\text{For } i_{max}, i_{max} \rightarrow R = \frac{mR}{n}$$

$$nR = mR$$

Heat and Power consumption →

$$\text{Heat} = \text{Power} \times \text{time}$$

$$H = I^2 RT \quad 1 \text{ kWh} = 3.6 \times 10^6 \text{ Joule.}$$

Bulb

$$P = \frac{V^2}{R}$$

(i) Series Connection



$$P = i^2 R$$

(iii) Series connection of resistive bulbs

$$\frac{1}{P_{\text{net}}} = \frac{1}{P_1} + \frac{1}{P_2}$$

(ii) Parallel Connection



$$P = \frac{V^2}{R}$$

(iv) Parallel connection of resistors / bulbs.

$$P_{\text{net}} = P_1 + P_2$$

- * Fundamental :- In series, resistance with higher value, have more power.
In parallel, resistance with lower value has more power.

Maximum Power Transfer

$$I = \frac{E}{R+r}, \text{ Power absorbed} \Rightarrow P = I^2 R = \left(\frac{E}{R+r} \right)^2 \times R$$

- * Power is maximum when $\Rightarrow r = R$.

Galvanometer (measures small amount of current in mA or μA).

denoted by I_g or I_{max} .

* Formula

use same logic
as in Ohm's law.

Ammeter (measures large amount of current).

$$* \boxed{I_g R_g = (I_A - I_g) R_s.}$$

- * To increase the range of galvanometer, a shunt resistance is connected parallel to it.

Voltmeter :- (measures p.d.)

This can be measured by connecting a resistance in series with galvanometer.

$$* \boxed{V = I_g (R_{\text{cr}} + R)}$$

** Topics :- Potentiometer and RC Circuit
Read from Notes.